
EEE339 Digital System Design with HDL

Assignment 1: Traffic Light Control

Student Name: Yi.Wang1902
Student ID: 1929718
Submission Date: Nov. 11th 2022

Contents

1 Task Description	2
1.1 Manual Mode	2
1.2 Auto Mode	3
1.3 Load Mode	3
1.4 Clock	4
2 User Interface	4
<u>2.1 Functions of toggle switch</u>	5
<u>2.2 Functions of LEDs</u>	5
<u>2.3 Functions of 7Segment Display</u>	5
3. ASM Chart	6
4 Simulation Results	7
5 Diagram of the synthesized circuit	11
Appendix A: Related pin assignment	12
Appendix B: Verilog Code	14

1 Task Description

There are four sets of traffic light required in the cross shown in Figure 1. Light 1 and 3 in direction A are controlled by the same signal. Light 2 and 4 in direction B are controlled by the same signal. There are four lights in each light set: turn left, red, yellow, and green. By default, the countdown time of each light is: $t_1 = 17s$ for green light, $t_2 = 6s$ for yellow light, $t_3 = 10s$ for turn left light. When the green light counts down to 5, the light will flash every 1 second. And the yellow light will always be flashing when turned on.

 


Figure 1: A Crossroad in this design

There are three modes in this system: manual, auto, and load. These modes are controlled by three toggle switches. The 'load mode' functions in parallel with the 'auto mode'. That is, when the system is in 'auto mode', a number can be loaded at the same time.

1.1 Manual Mode

In manual mode, the traffic light can be manually controlled by the police. There are four states in this mode. When M2M1M0 is '000', the light on path A is constant green and the light on path B is constant red. When M2M1M0 is '001', the light on path A is constant turn left and the light on path B is constant red. When M2M1M0 is '010', the light on path A is constant red and the light on path B is constant green. When M2M1M0 is '011', the light on path A is constant red and the light on path B is constant turn left. In this mode, the number on seven segment display is always 00.

The corresponding input control signal and output LED lights are also shown in Table 1.

Control Mode				
Mode	M2	M1	M0	Description
Manul	0	0	0	Path A Green; Path B Red
	0	0	1	Path A Left; Path B Red
	0	1	0	Path A Red; Path B Green
	0	1	1	Path A Red; Path B Left
Auto	1	0	0	Tansists from S1 to S8
Load	1	0	1	Load t1: Green light time
	1	1	0	Load t2: Yellow light time
	1	1	1	Load t3: turn left light time

Table 1: Control signals and related modes

1.2 Auto Mode

In auto mode, the lights on road A and B are turned on and off automatically. The transition table is shown in Table 2.

	M2M1M0	State	A	B	time
Manul	000		Green	Red	~
	001		Left	Red	~
	010		Red	Green	~
	011		Red	Left	~
Auto	100	S1	Green	Red	t1
		S2	Yellow	Red	t2
		S3	Left	Red	t3
		S4	Yellow	Red	t2
		S5	Red	Green	t1
		S6	Red	Yellow	t2
		S7	Red	Left	t3
		S8	Red	Yellow	t2

Table 2: Transition table in manual and auto mode

In the states S1 to S4, the LEDs on path A goes from Green to Yellow to Left and finally to Yellow, and the LEDs on path B is always Red in these four states. In the states S5 to S8, the LEDs on path B goes from Green to Yellow to Left and finally to Yellow, and the LEDs on path A is always Red in these four states. The corresponding default time durations are: $t1 = 17s$, $t2 = 6s$, $t3 = 10s$. When the green light counts down to 5, the LED will flash every 1 second. And the yellow light will always be flashing when turned on. The seven-segment display will also show the countdown number in auto mode. For example, to count the green light time $t1 = 17s$, the last two digits of the seven-segment display counts from 16 to 00, and the number changes every 1 second.

1.3 Load Mode

In load mode, five bits binary number can be loaded into countdown time $t1$ or $t2$ or $t3$. And the binary number to be loaded is controlled by five toggle switches: SW7 to SW3. The related input control signal and the countdown time are shown in Table 1. When M2M1M0 is '101', $t1$ could be changed. When M2M1M0 is '110', $t2$ could be changed. When M2M1M0 is '111', $t3$ could be changed. After the numbers are loaded, the traffic light will always function according to these

loaded times until the ‘preset’ switch is turned on.

1.4 Clock

In this system, a 27MHz internal clock signal is used. This signal will be transformed into a 1Hz signal by a module called ‘timeCounter’. The leftmost LEDR9 also flashes every one second to indicate the 1Hz clock.

2 User interface

The DE1 board and related functions of LEDs and switches are shown in Figure 2.

 


Figure 2: The DE1 board and related functions

2.1 Functions of toggle switched

Toggle Switch	name	function
SW[9]	rst	Reset the system to state S1 and the default time
SW[7]	L4	Input the binary represenatation of the loaded time
SW[6]	L3	
SW[5]	L2	
SW[4]	L1	
SW[3]	L0	Select Control Mode
SW[2]	M2	
SW[1]	M1	
SW[0]	M0	

SW[9] is the reset switch. When SW[9] is on, the state of auto mode returns to S1, and all the countdown time t1, t2, t3 returns to default.

SW[7] to SW[3] represents loaded binary number. For example, set SW[7] to SW[3] to '11001', and after M2M1M0 set the board to load mode, '25' will be loaded into the

corresponding countdown time.

SW[2], SW[1] and SW[0] represents the input mode control signal M2M1M0. Through toggling these three switches, the system can transit between 'Manual Mode', 'Auto Mode', and 'Load Mode'.

2.2 Functions of LEDs

LEDs	name	function
LEDR[3]	led[7]	Control the traffic light in direction A
LEDR[2]	led[6]	
LEDR[1]	led[4]	
LEDR[0]	led[5]	
LEDG[7]	led[3]	Control the traffic light in direction B
LEDG[6]	led[2]	
LEDG[5]	led[0]	
LEDG[4]	led[1]	
LEDR[9]	clk1	indicate the 1Hz clock

LEDR[3] to LEDR[0] controls the traffic light in direction A; and LEDG[7] to LEDG[4] controls the traffic light in direction B.

LEDR[9] indicate the 1HZ clock. It flashes every 1 second.

2.3 Functions of 7Segment Display

7Segment Display	name	function	7Segment Display	name	function
HEX0[0]	Ones	Control the ones digit of the 7 Segment Display on path A	HEX2[0]	Ones_add	Control the ones digit of the 7 Segment Display on path B
HEX0[1]			HEX2[1]		
HEX0[2]			HEX2[2]		
HEX0[3]			HEX2[3]		
HEX0[4]			HEX2[4]		
HEX0[5]			HEX2[5]		
HEX0[6]			HEX2[6]		
HEX1[0]	Tens	Control the tens digit of the 7 Segment Display on path A	HEX3[0]	Tens_add	Control the tens digit of the 7 Segment Display on path B
HEX1[1]			HEX3[1]		
HEX1[2]			HEX3[2]		
HEX1[3]			HEX3[3]		
HEX1[4]			HEX3[4]		
HEX1[5]			HEX3[5]		
HEX1[6]			HEX3[6]		

In auto mode, HEX0 and HEX1 can display the remaining countdown time in path A. HEX2 and HEX3 can display the remaining countdown time in path B. In manual mode, the 7Segment Display will all display 0.

HEX0 and HEX2 represents the tens digit of the countdown time. HEX1 and HEX3 represents the tens digit of the countdown time

3 ASM Chart

The ASM chart in auto mode is shown in Figure 3.


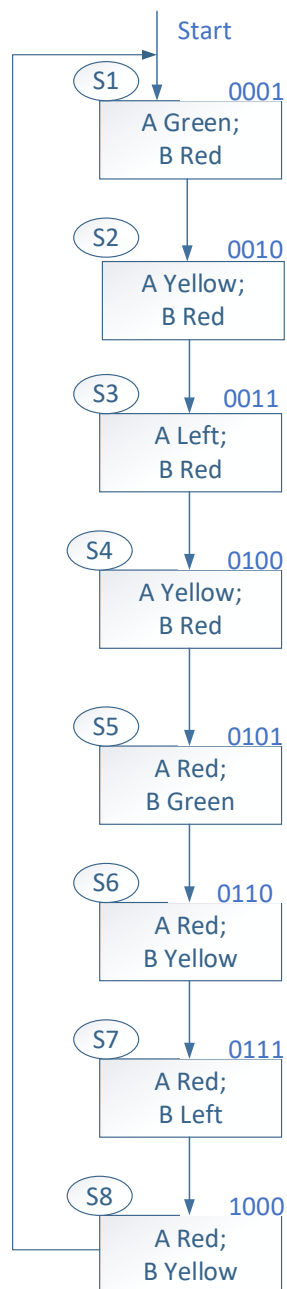
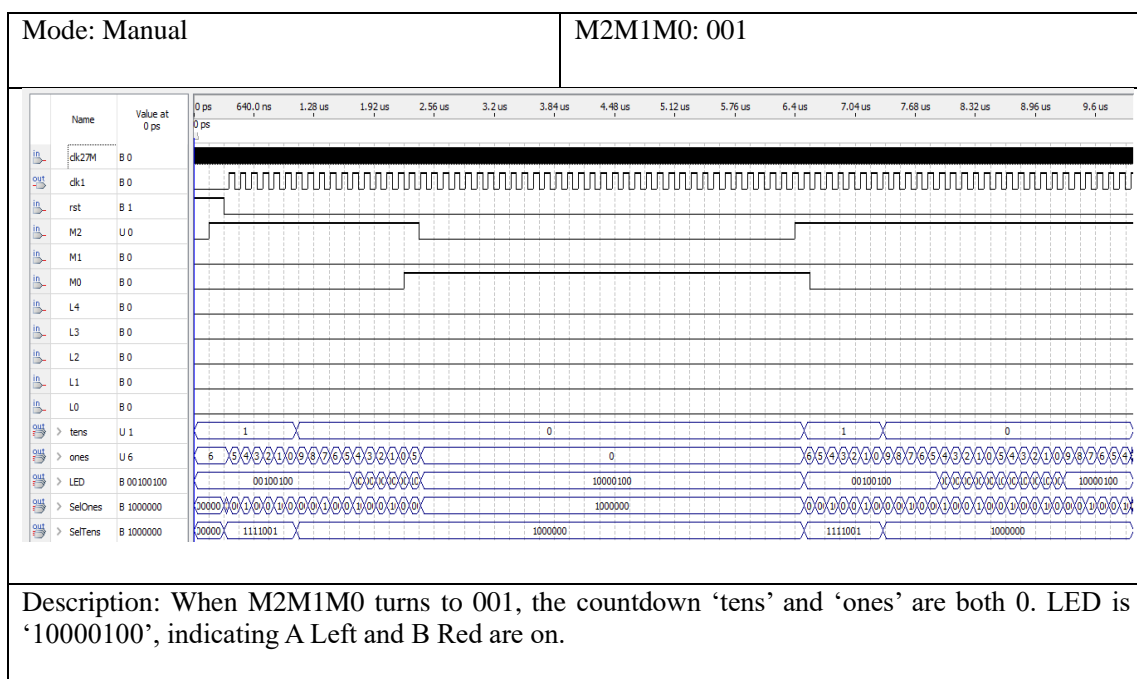


Figure 3: ASM chart in auto mode


4 Simulation Result

To better simulate the traffic light system, the 'timeCounter' module and the input 27MHz clock signals are adjusted so that the period of clk1 is 120ns. 'rst' is the reset signal. 'M2M1M0' are the mode control signals. 'L4 L3 L2 L1 L0' represents the number to be loaded into the system. 'tens' and 'ones' represent the corresponding digits of t1, t2, and t3. LED represents the eight traffic lights: A Left, A Red, A Green, A Yellow, B Left, B Red, B Green, B Yellow. 'SelOnes' controls the ones digit on the 7Segment Display, and 'SelTens' controls the tens digit on the 7Segment Display.

 

Mode: Manual


M2M1M0: 010

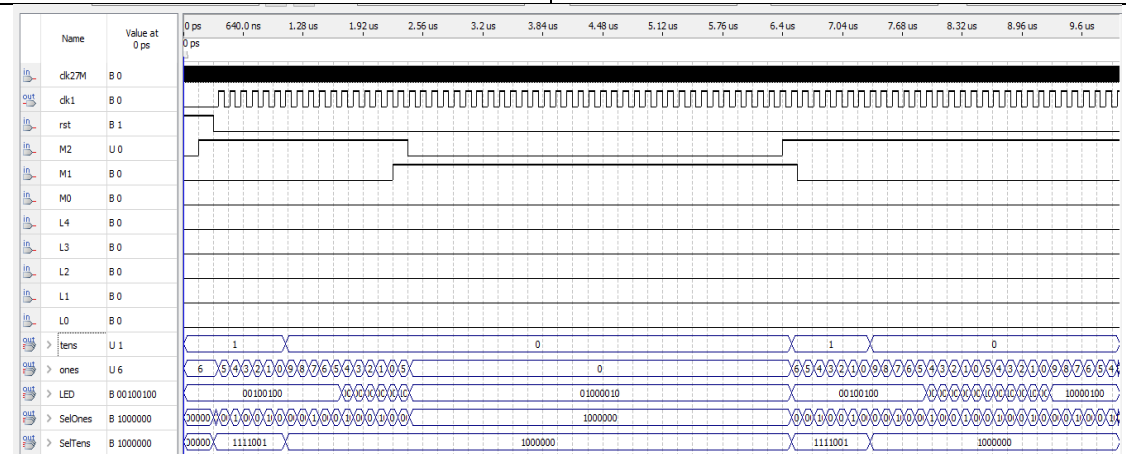


Description: When M2M1M0 turns to 010, the countdown 'tens' and 'ones' are both 0. LED is '01000010', indicating A Red and B Green are on.

Mode: Manual

M2M1M0: 011

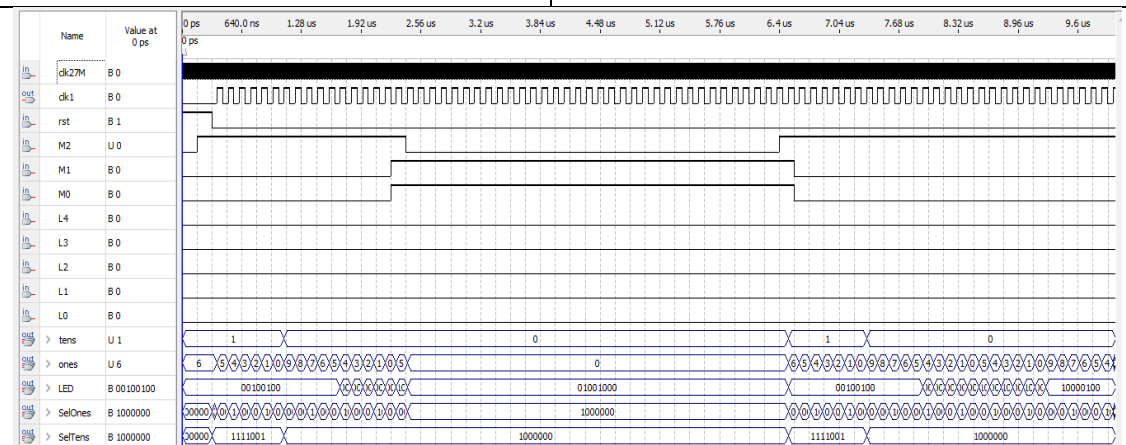

 Description: When M2M1M0 turns to 000, the countdown 'tens' and 'ones' are both 0. LED is '01001000', indicating A Green and B Left are on.





Appendix A: Related pin assignments

Toggle switches	Signal Name	FPGA Pin No.	Description
	SW[0]	PIN_L22	Toggle Switch[0]
	SW[1]	PIN_L21	Toggle Switch[1]
	SW[2]	PIN_M22	Toggle Switch[2]
	SW[3]	PIN_V12	Toggle Switch[3]
	SW[4]	PIN_W12	Toggle Switch[4]
	SW[5]	PIN_U12	Toggle Switch[5]
	SW[6]	PIN_U11	Toggle Switch[6]
	SW[7]	PIN_M2	Toggle Switch[7]
	SW[8]	PIN_M1	Toggle Switch[8]
	SW[9]	PIN_L2	Toggle Switch[9]
LEDs	Signal Name	FPGA Pin No.	Description
	LEDR[0]	PIN_R20	LED Red[0]
	LEDR[1]	PIN_R19	LED Red[1]
	LEDR[2]	PIN_U19	LED Red[2]
	LEDR[3]	PIN_Y19	LED Red[3]
	LEDR[4]	PIN_T18	LED Red[4]
	LEDR[5]	PIN_V19	LED Red[5]
	LEDR[6]	PIN_Y18	LED Red[6]
	LEDR[7]	PIN_U18	LED Red[7]
	LEDR[8]	PIN_R18	LED Red[8]
	LEDR[9]	PIN_R17	LED Red[9]
	LEDG[0]	PIN_U22	LED Green[0]
	LEDG[1]	PIN_U21	LED Green[1]
	LEDG[2]	PIN_V22	LED Green[2]
	LEDG[3]	PIN_V21	LED Green[3]
	LEDG[4]	PIN_W22	LED Green[4]
	LEDG[5]	PIN_W21	LED Green[5]
	LEDG[6]	PIN_Y22	LED Green[6]
	LEDG[7]	PIN_Y21	LED Green[7]

7Segment Display	Signal Name	FPGA Pin No.	Description
	HEX0[0]	PIN_J2	Seven Segment Digit 0[0]
	HEX0[1]	PIN_J1	Seven Segment Digit 0[1]
	HEX0[2]	PIN_H2	Seven Segment Digit 0[2]
	HEX0[3]	PIN_H1	Seven Segment Digit 0[3]
	HEX0[4]	PIN_F2	Seven Segment Digit 0[4]
	HEX0[5]	PIN_F1	Seven Segment Digit 0[5]
	HEX0[6]	PIN_E2	Seven Segment Digit 0[6]
	HEX1[0]	PIN_E1	Seven Segment Digit 1[0]
	HEX1[1]	PIN_H6	Seven Segment Digit 1[1]
	HEX1[2]	PIN_H5	Seven Segment Digit 1[2]
	HEX1[3]	PIN_H4	Seven Segment Digit 1[3]
	HEX1[4]	PIN_G3	Seven Segment Digit 1[4]
	HEX1[5]	PIN_D2	Seven Segment Digit 1[5]
	HEX1[6]	PIN_D1	Seven Segment Digit 1[6]
	HEX2[0]	PIN_G5	Seven Segment Digit 2[0]
	HEX2[1]	PIN_G6	Seven Segment Digit 2[1]
	HEX2[2]	PIN_C2	Seven Segment Digit 2[2]
	HEX2[3]	PIN_C1	Seven Segment Digit 2[3]
	HEX2[4]	PIN_E3	Seven Segment Digit 2[4]
	HEX2[5]	PIN_E4	Seven Segment Digit 2[5]
	HEX2[6]	PIN_D3	Seven Segment Digit 2[6]
	HEX3[0]	PIN_F4	Seven Segment Digit 3[0]
	HEX3[1]	PIN_D5	Seven Segment Digit 3[1]
	HEX3[2]	PIN_D6	Seven Segment Digit 3[2]
	HEX3[3]	PIN_J4	Seven Segment Digit 3[3]
	HEX3[4]	PIN_L8	Seven Segment Digit 3[4]
	HEX3[5]	PIN_F3	Seven Segment Digit 3[5]
	HEX3[6]	PIN_D4	Seven Segment Digit 3[6]
Clock input	Signal Name	FPGA Pin No.	Description
	CLOCK_27	PIN_D12, PIN_E12	27 MHz clock input
	CLOCK_50	PIN_L1	50 MHz clock input
	CLOCK_24	PIN_A12, PIN_B12	24 MHz clock input from USB Blaster
	EXT_CLOCK	PIN_M21	External (SMA) clock input

Appendix B: Verilog Code

```

module timeCounter (clk27M, rst, clk1);    //27M Hz clock frequency to 1Hz
    input    clk27M, rst;
    output   clk1;
    reg [24:0]j;
    reg clk1;
    always@ (posedge clk27M or posedge rst)
        if (rst)
            begin
                clk1 <= 0;
                j <= 0;
            end
        //else if (j == 13500000)
        else if (j == 5)
            begin
                j <= 0;
                clk1 <= ~clk1;
            end
        else
            j <= j + 1;
endmodule

module control (rst, clk1,
                M2, M1, M0,    //control mode
                L4, L3, L2, L1, L0,    //load number
                led,           //traffic light
                Tens,          //ns seg tens
                Ones,          //ns seg ones
                Tens_add,Ones_add
                );
    input rst, clk1, M2, M1, M0, L4, L3, L2, L1, L0;

    output [7:0] led;           //"aL,aR,aG,aY; bL,bR,bG,bY"
    output [3:0] Tens, Ones;    //for 7 segment
    output [3:0] Tens_add, Ones_add;    //for 7 segment
    reg [7:0] led;
    reg [3:0] Tens, Ones;
    reg [3:0] Tens_add, Ones_add;
    wire [2:0]a;                //control index
    wire [4:0]L;
    reg [3:0] state;
    parameter S1 = 4'b0001,
               S2 = 4'b0010,
               S3 = 4'b0011,
               S4 = 4'b0100,
               S5 = 4'b0101,
               S6 = 4'b0110,
               S7 = 4'b0111,
               S8 = 4'b1000,
               S9 = 4'b1001,
               S10= 4'b1010,
               S11= 4'b1011,
               S12= 4'b1100;

    reg [3:0]t1_Tens = 4'b0001, t1_Ones = 4'b0110,    //Green light time

```

```

                t2_Tens = 4'b0000, t2_Ones = 4'b0101, //Yellow light time
                t3_Tens = 4'b0000, t3_Ones = 4'b1001; //turn left time
reg [3:0]t_Tens_add = 4'b0011, t_Ones_add = 4'b1000;
assign a = {M2, M1, M0};
assign L = {L4, L3, L2, L1, L0};

always @(posedge clk1 or posedge rst)
    if (rst) //initialize
        begin
            t1_Tens = 4'b0001; t1_Ones = 4'b0110; //Green light time
            t2_Tens = 4'b0000; t2_Ones = 4'b0101; //Yellow light time
            t3_Tens = 4'b0000; t3_Ones = 4'b1001;
        end
    else if (a == 3'b111) //load Turn Left time t3
        begin
            case (L)
                //5'b00000:begin t3_Tens = 0; t3_Ones = 0; end
                5'b00001:begin t3_Tens = 0; t3_Ones = 1; end
                5'b00010:begin t3_Tens = 0; t3_Ones = 2; end
                5'b00011:begin t3_Tens = 0; t3_Ones = 3; end
                5'b00100:begin t3_Tens = 0; t3_Ones = 4; end
                5'b00101:begin t3_Tens = 0; t3_Ones = 5; end
                5'b00110:begin t3_Tens = 0; t3_Ones = 6; end
                5'b00111:begin t3_Tens = 0; t3_Ones = 7; end
                5'b01000:begin t3_Tens = 0; t3_Ones = 8; end
                5'b01001:begin t3_Tens = 0; t3_Ones = 9; end
                5'b01010:begin t3_Tens = 1; t3_Ones = 0; end
                5'b01011:begin t3_Tens = 1; t3_Ones = 1; end
                5'b01100:begin t3_Tens = 1; t3_Ones = 2; end
                5'b01101:begin t3_Tens = 1; t3_Ones = 3; end
                5'b01110:begin t3_Tens = 1; t3_Ones = 4; end
                5'b01111:begin t3_Tens = 1; t3_Ones = 5; end

                5'b10000:begin t3_Tens = 1; t3_Ones = 6; end
                5'b10001:begin t3_Tens = 1; t3_Ones = 7; end
                5'b10010:begin t3_Tens = 1; t3_Ones = 8; end
                5'b10011:begin t3_Tens = 1; t3_Ones = 9; end
                5'b10100:begin t3_Tens = 2; t3_Ones = 0; end
                5'b10101:begin t3_Tens = 2; t3_Ones = 1; end
                5'b10110:begin t3_Tens = 2; t3_Ones = 2; end
                5'b10111:begin t3_Tens = 2; t3_Ones = 3; end
                5'b11000:begin t3_Tens = 2; t3_Ones = 4; end
                5'b11001:begin t3_Tens = 2; t3_Ones = 5; end
                5'b11010:begin t3_Tens = 2; t3_Ones = 6; end
                5'b11011:begin t3_Tens = 2; t3_Ones = 7; end
                5'b11100:begin t3_Tens = 2; t3_Ones = 8; end
                5'b11101:begin t3_Tens = 2; t3_Ones = 9; end
                5'b11110:begin t3_Tens = 3; t3_Ones = 0; end
                5'b11111:begin t3_Tens = 3; t3_Ones = 1; end
                default:begin t3_Tens = 0; t3_Ones = 9; end
            endcase
        end
    else if (a == 3'b110) //load Yellow light time t2
        begin
            case (L)
                //5'b00000:begin t2_Tens = 0; t2_Ones = 0; end
                5'b00001:begin t2_Tens = 0; t2_Ones = 1; end

```



```

5'b00010:begin t2_Tens = 0; t2_Ones = 2; end
5'b00011:begin t2_Tens = 0; t2_Ones = 3; end
5'b00100:begin t2_Tens = 0; t2_Ones = 4; end
5'b00101:begin t2_Tens = 0; t2_Ones = 5; end
5'b00110:begin t2_Tens = 0; t2_Ones = 6; end
5'b00111:begin t2_Tens = 0; t2_Ones = 7; end
5'b01000:begin t2_Tens = 0; t2_Ones = 8; end
5'b01001:begin t2_Tens = 0; t2_Ones = 9; end
5'b01010:begin t2_Tens = 1; t2_Ones = 0; end
5'b01011:begin t2_Tens = 1; t2_Ones = 1; end
5'b01100:begin t2_Tens = 1; t2_Ones = 2; end
5'b01101:begin t2_Tens = 1; t2_Ones = 3; end
5'b01110:begin t2_Tens = 1; t2_Ones = 4; end
5'b01111:begin t2_Tens = 1; t2_Ones = 5; end

5'b10000:begin t2_Tens = 1; t2_Ones = 6; end
5'b10001:begin t2_Tens = 1; t2_Ones = 7; end
5'b10010:begin t2_Tens = 1; t2_Ones = 8; end
5'b10011:begin t2_Tens = 1; t2_Ones = 9; end
5'b10100:begin t2_Tens = 2; t2_Ones = 0; end
5'b10101:begin t2_Tens = 2; t2_Ones = 1; end
5'b10110:begin t2_Tens = 2; t2_Ones = 2; end
5'b10111:begin t2_Tens = 2; t2_Ones = 3; end
5'b11000:begin t2_Tens = 2; t2_Ones = 4; end
5'b11001:begin t2_Tens = 2; t2_Ones = 5; end
5'b11010:begin t2_Tens = 2; t2_Ones = 6; end
5'b11011:begin t2_Tens = 2; t2_Ones = 7; end
5'b11100:begin t2_Tens = 2; t2_Ones = 8; end
5'b11101:begin t2_Tens = 2; t2_Ones = 9; end
5'b11110:begin t2_Tens = 3; t2_Ones = 0; end
5'b11111:begin t2_Tens = 3; t2_Ones = 1; end
default:begin t2_Tens = 0; t2_Ones = 5; end
endcase
end

else if (a == 3'b101) //load Green time t1
begin
case (L)
//5'b00000:begin t1_Tens = 0; t1_Ones = 0; end
5'b00001:begin t1_Tens = 0; t1_Ones = 1; end
5'b00010:begin t1_Tens = 0; t1_Ones = 2; end
5'b00011:begin t1_Tens = 0; t1_Ones = 3; end
5'b00100:begin t1_Tens = 0; t1_Ones = 4; end
5'b00101:begin t1_Tens = 0; t1_Ones = 5; end
5'b00110:begin t1_Tens = 0; t1_Ones = 6; end
5'b00111:begin t1_Tens = 0; t1_Ones = 7; end
5'b01000:begin t1_Tens = 0; t1_Ones = 8; end
5'b01001:begin t1_Tens = 0; t1_Ones = 9; end
5'b01010:begin t1_Tens = 1; t1_Ones = 0; end
5'b01011:begin t1_Tens = 1; t1_Ones = 1; end
5'b01100:begin t1_Tens = 1; t1_Ones = 2; end
5'b01101:begin t1_Tens = 1; t1_Ones = 3; end
5'b01110:begin t1_Tens = 1; t1_Ones = 4; end
5'b01111:begin t1_Tens = 1; t1_Ones = 5; end

5'b10000:begin t1_Tens = 1; t1_Ones = 6; end
5'b10001:begin t1_Tens = 1; t1_Ones = 7; end
5'b10010:begin t1_Tens = 1; t1_Ones = 8; end

```

```

5'b10011:begin t1_Tens = 1; t1_Ones = 9; end
5'b10100:begin t1_Tens = 2; t1_Ones = 0; end
5'b10101:begin t1_Tens = 2; t1_Ones = 1; end
5'b10110:begin t1_Tens = 2; t1_Ones = 2; end
5'b10111:begin t1_Tens = 2; t1_Ones = 3; end
5'b11000:begin t1_Tens = 2; t1_Ones = 4; end
5'b11001:begin t1_Tens = 2; t1_Ones = 5; end
5'b11010:begin t1_Tens = 2; t1_Ones = 6; end
5'b11011:begin t1_Tens = 2; t1_Ones = 7; end
5'b11100:begin t1_Tens = 2; t1_Ones = 8; end
5'b11101:begin t1_Tens = 2; t1_Ones = 9; end
5'b11110:begin t1_Tens = 3; t1_Ones = 0; end
5'b11111:begin t1_Tens = 3; t1_Ones = 1; end
default:begin t1_Tens = 1; t1_Ones = 6; end
endcase
end

always@ (posedge clk1 or posedge rst)
if (rst)
begin
state <= S1;
led <= 8'b00100100; //aG bR
Tens <= t1_Tens; Ones <= t1_Ones; //t=40s
end
else
begin
casex (a)
3'b000: //manual 1
begin
state <= S9;
led <= 8'b00100100; //aG bR
Tens <= 4'd0; Ones <= 4'd0;
end
3'b001: //msnual 2
begin
state <= S10;
led <= 8'b10000100; //aL bR
Tens <= 4'd0; Ones <= 4'd0;
end
3'b010: //manual 3
begin
state <= S11;
led <= 8'b01000010; //aR bG
Tens <= 4'd0; Ones <= 4'd0;
end
3'b011: //manual 4
begin
state <= S12;
led <= 8'b01001000; //aR bL
Tens <= 4'd0; Ones <= 4'd0;
end
3'b1xx: //auto 5
begin
case (state)
S1: if (Tens==0 && Ones==0) //if both ones and tens are 0, switch to next state
begin
state <= S2;

```

```

        led <= 8'b00010100; //aY bR
        Tens <= t2_Tens;    Ones <= t2_Ones;
    end
    else if (Ones)    //ones are not 0
    begin
        Ones <= Ones - 1;
        if (Ones <= 5 && Tens == 0)
            begin
                led[5] <= ~led[5];    //A Green flash
            end
        end
    end
    else if (Tens)    //tens are not 0
    begin
        Ones <= 9;
        Tens <= Tens - 1;
    end
    S2: if (Tens==0 && Ones==0)    //if both ones and tens are 0, switch to next state
    begin
        state <= S3;
        led <= 8'b10000100; //aL bR
        Tens <= t3_Tens;    Ones <= t3_Ones;
    end
    else if (Ones)    //ones are not 0
    begin
        led[4] <= ~led[4];    //A Yellow flash
        led[5] <= 0;
        Ones <= Ones - 1;
    end
    else if (Tens)    //tens are not 0
    begin
        Ones <= 9;
        Tens <= Tens - 1;
    end
    S3: if (Tens==0 && Ones==0)    //if both ones and tens are 0, switch to next state
    begin
        state <= S4;
        led <= 8'b00010100; //aY bR 5s
        Tens <= t2_Tens;    Ones <= t2_Ones;
    end
    else if (Ones)    //ones are not 0
    begin
        Ones <= Ones - 1;
    end
    else if (Tens)    //tens are not 0
    begin
        Ones <= 9;
        Tens <= Tens - 1;
    end
    S4: if (Tens==0 && Ones==0)    //if both ones and tens are 0, switch to next state
    begin
        state <= S5;
        led <= 8'b01000010; //aR bG 40s
        Tens <= t1_Tens;    Ones <= t1_Ones;
    end
    else if (Ones)    //ones are not 0
    begin
        led[4] <= ~led[4];    //A Yellow flash

```

```

        led[7] <= 0;
        Ones <= Ones - 1;
    end
    else if (Tens)    //tens are not 0
    begin
        Ones <= 9;
        Tens <= Tens - 1;
    end
S5: if (Tens==0 && Ones==0)    //if both ones and tens are 0, switch to next state
    begin
        state <= S6;
        led <= 8'b01000001; //aR bY 5s
        Tens <= t2_Tens;    Ones <= t2_Ones;
    end
    else if (Ones)    //ones are not 0
    begin
        Ones <= Ones - 1;
        if (Ones <= 5 && Tens == 0)
            begin
                led[1] <= ~led[1];    //B Green flash
            end
        end
    else if (Tens)    //tens are not 0
    begin
        Ones <= 9;
        Tens <= Tens - 1;
    end
S6: if (Tens==0 && Ones==0)    //if both ones and tens are 0, switch to next state
    begin
        state <= S7;
        led <= 8'b01001000; //aR bL 10s
        Tens <= t3_Tens;    Ones <= t3_Ones;
    end
    else if (Ones)    //ones are not 0
    begin
        led[0] <= ~led[0];    //B Yellow flash
        led[1] <= 0;
        Ones <= Ones - 1;
    end
    else if (Tens)    //tens are not 0
    begin
        Ones <= 9;
        Tens <= Tens - 1;
    end
S7: if (Tens==0 && Ones==0)    //if both ones and tens are 0, switch to next state
    begin
        state <= S8;
        led <= 8'b01000001; //aR bY 5s
        Tens <= t2_Tens;    Ones <= t2_Ones;
    end
    else if (Ones)    //ones are not 0
    begin
        Ones <= Ones - 1;
    end
    else if (Tens)    //tens are not 0
    begin
        Ones <= 9;

```

```

        Tens <= Tens - 1;
    end
    S8: if (Tens==0 && Ones==0) //if both ones and tens are 0, switch to next state
    begin
        state <= S1;
        led <= 8'b00100100; //aG bR 40s
        Tens <= t1_Tens;    Ones <= t1_Ones;
    end
    else if (Ones) //ones are not 0
    begin
        led[0] <= ~led[0];    //B Yellow flash
        led[3] <= 0;
        Ones <= Ones - 1;
    end
    else if (Tens) //tens are not 0
    begin
        Ones <= 9;
        Tens <= Tens - 1;
    end
    default: //entrance state S1
    begin
        state <= S1;
        led <= 8'b00100100; //aG bR 40s
        Tens <= t1_Tens;    Ones <= t1_Ones;
    end
    endcase
end
endcase
end

always@ (posedge clk1 or posedge rst)
if (rst)
begin
    Tens_add <= t_Tens_add; Ones_add <= t_Ones_add; //t=40s
end
else
begin
    casex (a)
        3'b000: //manual 1
        begin
            Tens_add <= 4'd0;    Ones_add <= 4'd0;
        end
        3'b001: //msnual 2
        begin
            Tens_add <= 4'd0;    Ones_add <= 4'd0;
        end
        3'b010: //manual 3
        begin
            Tens_add <= 4'd0;    Ones_add <= 4'd0;
        end
        3'b011: //manual 4
        begin
            Tens_add <= 4'd0;    Ones_add <= 4'd0;
        end
        3'b1xx: //auto 5
        begin
            if (Tens_add==0 && Ones_add==0) //if both ones and tens are 0, switch to

```

```

next state
    begin
        Tens_add <= t_Tens_add; Ones_add <= t_Ones_add;
    end
    else if (Ones_add)    //ones are not 0
    begin
        Ones_add <= Ones_add - 1;
    end
    else if (Tens_add)    //tens are not 0
    begin
        Ones_add <= 9;
        Tens_add <= Tens_add - 1;
    end

    end
endcase
end

endmodule

```

```

module Seg7 (rst, clk, Tens, Ones, selOnes, selTens);
    input rst, clk;          //reset, clock
    input [3:0]Tens, Ones; //traffic light count down
    output [6:0]selOnes;
    output [6:0]selTens;

    reg [6:0]selOnes;
    reg [6:0]selTens;
    reg [13:0]nonDisplay;

    always@(Ones or rst)
    begin
        if (rst)
            selOnes = 7'b0111111;
        else
            begin
                case (Ones)
                    4'b0000:selOnes = 7'b0111111;
                    4'b0001:selOnes = 7'b0000110;
                    4'b0010:selOnes = 7'b1011011;
                    4'b0011:selOnes = 7'b1001111;
                    4'b0100:selOnes = 7'b1100110;
                    4'b0101:selOnes = 7'b1101101;
                    4'b0110:selOnes = 7'b1111101;
                    4'b0111:selOnes = 7'b0000111;
                    4'b1000:selOnes = 7'b1111111;
                    4'b1001:selOnes = 7'b1101111;
                    default:selOnes = 7'b0111111;
                endcase
            end
    end

    always@(Tens or rst)
    begin
        if (rst)
            selTens = 7'b0111111;
    end

```

```

        else
            begin
                case (Tens)
                    4'b0000:selTens = 7'b01111111;
                    4'b0001:selTens = 7'b00001110;
                    4'b0010:selTens = 7'b1011011;
                    4'b0011:selTens = 7'b1001111;
                    4'b0100:selTens = 7'b11001110;
                    4'b0101:selTens = 7'b1101101;
                    4'b0110:selTens = 7'b1111101;
                    4'b0111:selTens = 7'b0000111;
                    4'b1000:selTens = 7'b1111111;
                    4'b1001:selTens = 7'b1101111;
                    default:selTens = 7'b0111111;
                endcase
            end
        end
    end
endmodule

module Seg7_add (rst, clk, Tens_add, Ones_add, selOnes_add, selTens_add);
    input rst, clk;          //reset, clock
    input [3:0]Tens_add, Ones_add; //traffic light count down
    output [6:0]selOnes_add;
    output [6:0]selTens_add;

    reg [6:0]selOnes_add;
    reg [6:0]selTens_add;

    always@(Ones_add or rst)
        begin
            if (rst)
                selOnes_add = 7'b0111111;
            else
                begin
                    case (Ones_add)
                        4'b0000:selOnes_add = 7'b0111111;
                        4'b0001:selOnes_add = 7'b00001110;
                        4'b0010:selOnes_add = 7'b1011011;
                        4'b0011:selOnes_add = 7'b1001111;
                        4'b0100:selOnes_add = 7'b11001110;
                        4'b0101:selOnes_add = 7'b1101101;
                        4'b0110:selOnes_add = 7'b1111101;
                        4'b0111:selOnes_add = 7'b0000111;
                        4'b1000:selOnes_add = 7'b1111111;
                        4'b1001:selOnes_add = 7'b1101111;
                        default:selOnes_add = 7'b0111111;
                    endcase
                end
            end

    always@(Tens_add or rst)
        begin
            if (rst)
                selTens_add = 7'b0111111;
            else
                begin
                    case (Tens_add)

```

```
        4'b0000:selTens_add = 7'b01111111;  
        4'b0001:selTens_add = 7'b00001110;  
        4'b0010:selTens_add = 7'b10110111;  
        4'b0011:selTens_add = 7'b10011111;  
        4'b0100:selTens_add = 7'b11001110;  
        4'b0101:selTens_add = 7'b11011011;  
        4'b0110:selTens_add = 7'b11111011;  
        4'b0111:selTens_add = 7'b00001111;  
        4'b1000:selTens_add = 7'b11111111;  
        4'b1001:selTens_add = 7'b11011111;  
        default:selTens_add = 7'b01111111;  
    endcase  
end  
end  
endmodule
```